

Roll No.....

Total No. of Units : 03

Total No. of Printed Pages : 03

Code No. : 03/301

Third Semester Examination, Dec. 2018

M.Sc. PHYSICS

Paper - III

(SPECIAL PAPER I - ELECTRONICS)

Time : 3 Hrs.

Max. Marks : 80

- Part A and B of each question in each unit consist of very short answer type questions which are to be answered in one or two sentences.  
Part C (Short answer type) of each question will be answered in 200-250 words.  
Part D (Long answer type) of each question should be answered within the word limit 400-450.

**Unit - I**

Q.1 A. What is function of Differential amplifier? (2)

Q.1 B. Write one application of Balanced output differential amplifier. (2)

Q.1 C. Explain DC analysis of Dual Input-Balanced output differential Amplifier with its circuit diagram. (4)

**OR**

Explain constant current bias.

Q.1 D. Draw and explain circuit of FET differential amplifier and explain its DC and AC analysis. (12)

**P.T.O.**

(2)

Code No. : 03/301

**OR**

Draw and explain circuit diagram of Cascade differential amplifier.

**Unit - II**

Q.2 A. What is inverting amplifier? (2)

Q.2 B. What is feedback? (2)

Q.2 C. Write analysis of OP-AMP equivalent circuit. (4)

**OR**

Explain input offset voltage and input offset current.

Q.2 D. Draw circuit and explain working of voltage follower. (12)

**OR**

Draw and explain common mode configuration also explain CMRR.

**Unit - III**

Q.3 A. Write principle of vibrator. (2)

Q.3 B. What is clipping? (2)

Q.3 C. Explain working of OP-AMP as DC Amplifier. (4)

**OR**

How OP-AMP works as Summing Amplifier.

Q.3 D. Draw circuit diagram and explain working of frequency to voltage converter. (12)

(3)

Code No. : 03/301

**OR**

What is multivibrator? Explain working of mono-stable multivibrator.

**Unit - IV**

Q.4 A. What is square signal? (2)

Q.4 B. What do you mean by filtration? (2)

Q.4 C. Explain working of phase shifter. (4)

**OR**

What is narrow band reject filter?

Q.4 D. Draw circuit and explain working of First order high pass Butterworth filter. (12)

**OR**

Write principle of oscillator. Explain circuit and working of Wein-Bridge oscillator.

---X---